

# **COMP3222/9222 Digital Circuits & Systems**

Assignment Project Exam Help

## **5. Flip-flops, Registers, Counters**

<https://tutorcs.com>

WeChat: cstutorcs

# Objectives

- Learn about logic circuits that store information
  - Flip-flops that store a single bit
  - Registers that store multiple bits
  - Shift registers that shift the contents of the register
  - Counters of various types
- VHDL constructs used to implement storage elements


Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs
 
# Why we need circuits with memory


- Consider an alarm system that is required to remain activated when triggered, even when the cause for triggering has ceased



- Here, the *Reset* signal is intended to provide a means of switching off the alarm
 
# How do we create a memory element?

- Use feedback to “trap” a value
- Consider a simple cyclic circuit comprising two inverters





WeChat: cstutorcs


- The circuit has two stable states
- But there is no way of changing from one state to the other

# A controlled memory element

0 = preserve current state

 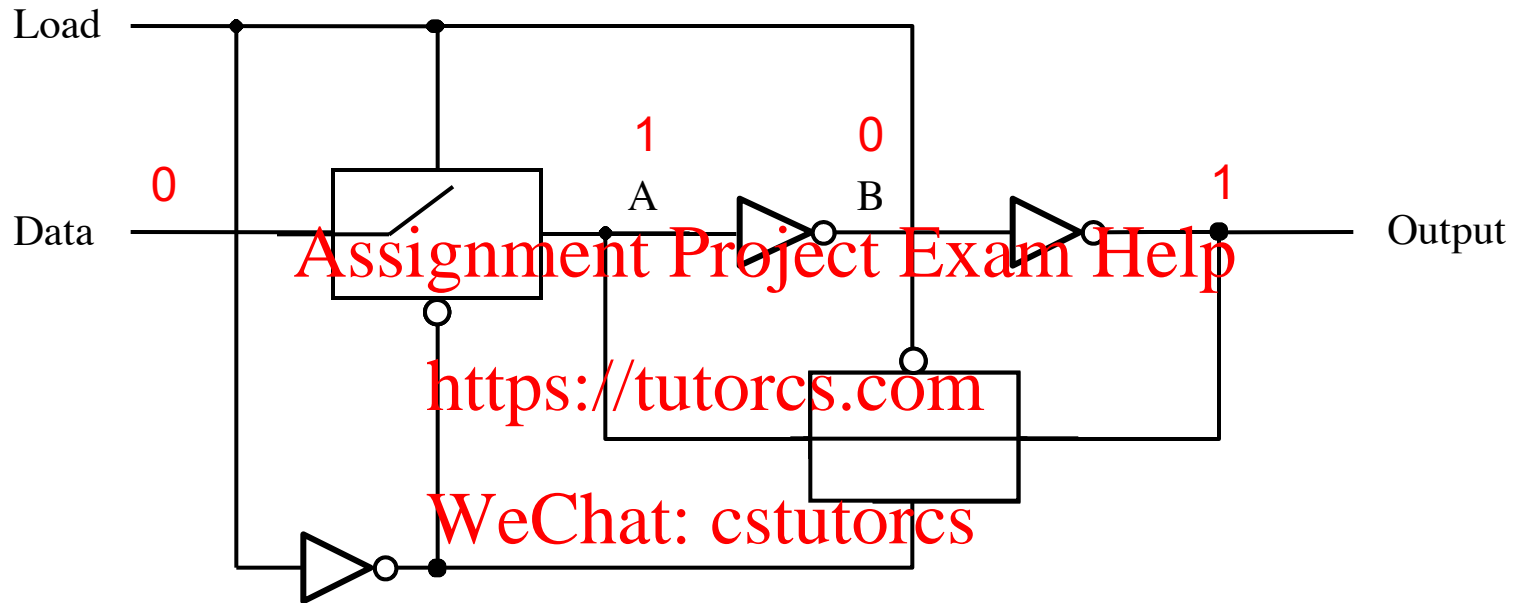

# A memory element with NOR gates

 


A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

WeChat: cstutorcs

- When both *Set* and *Reset* are 0, the state, *Q*, is preserved
- $Set = 1, Reset = 0 \Rightarrow Q = 1$
- $Set = 0, Reset = 1 \Rightarrow Q = 0$
- Known as a *latch*

 
# Basic latch using cross-coupled NOR gates



Assignment Project Exam Help

(a) Conventional circuit diagram


(b) Characteristic table

 



Oscillatory behaviour which settles to a final state that depends upon the relative speed of gates and wires
 
# Gated SR latch

- A control input ( $Clk$ ) acts to enable state changes



  
Illegal input condition as outputs are supposed to be complements of each other




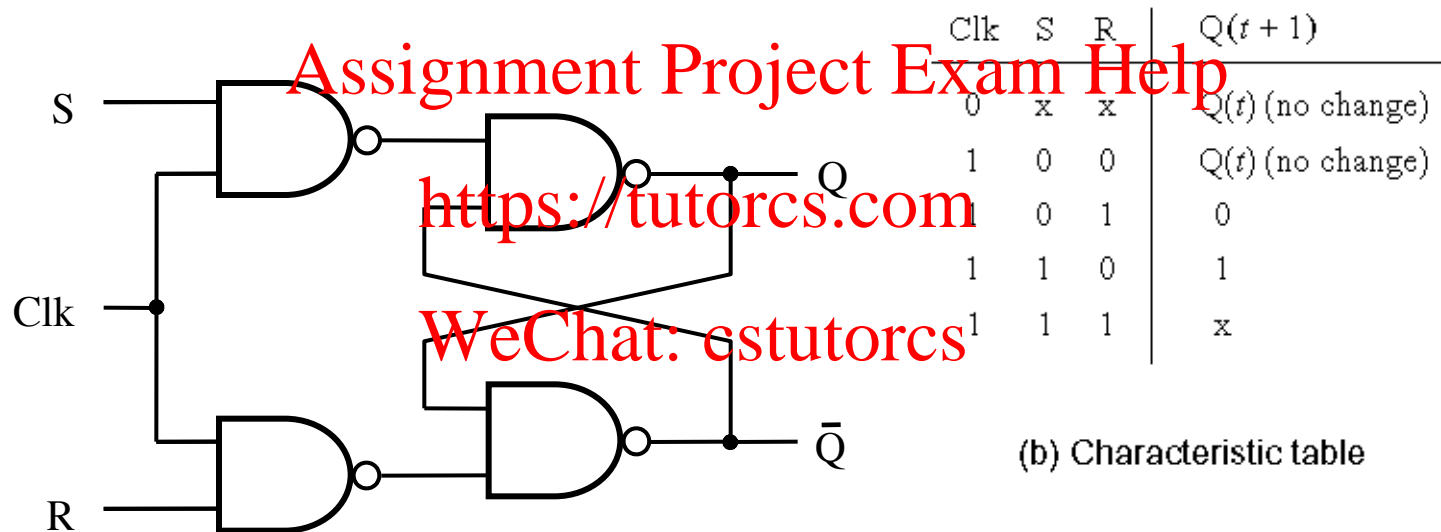
# Gated SR latch with NAND gates

- More usual configuration as it uses less transistors
  - Has exactly the same characteristic table
  - Note that S & R inputs are flipped about wrt the outputs






Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Characteristic table

A	B	A NAND B
0	0	1
0	1	1
1	0	1
1	1	0

   
# Gated D latch

- Eliminates the illegal input combination  $S = R = 1$
- Useful for storing a data bit



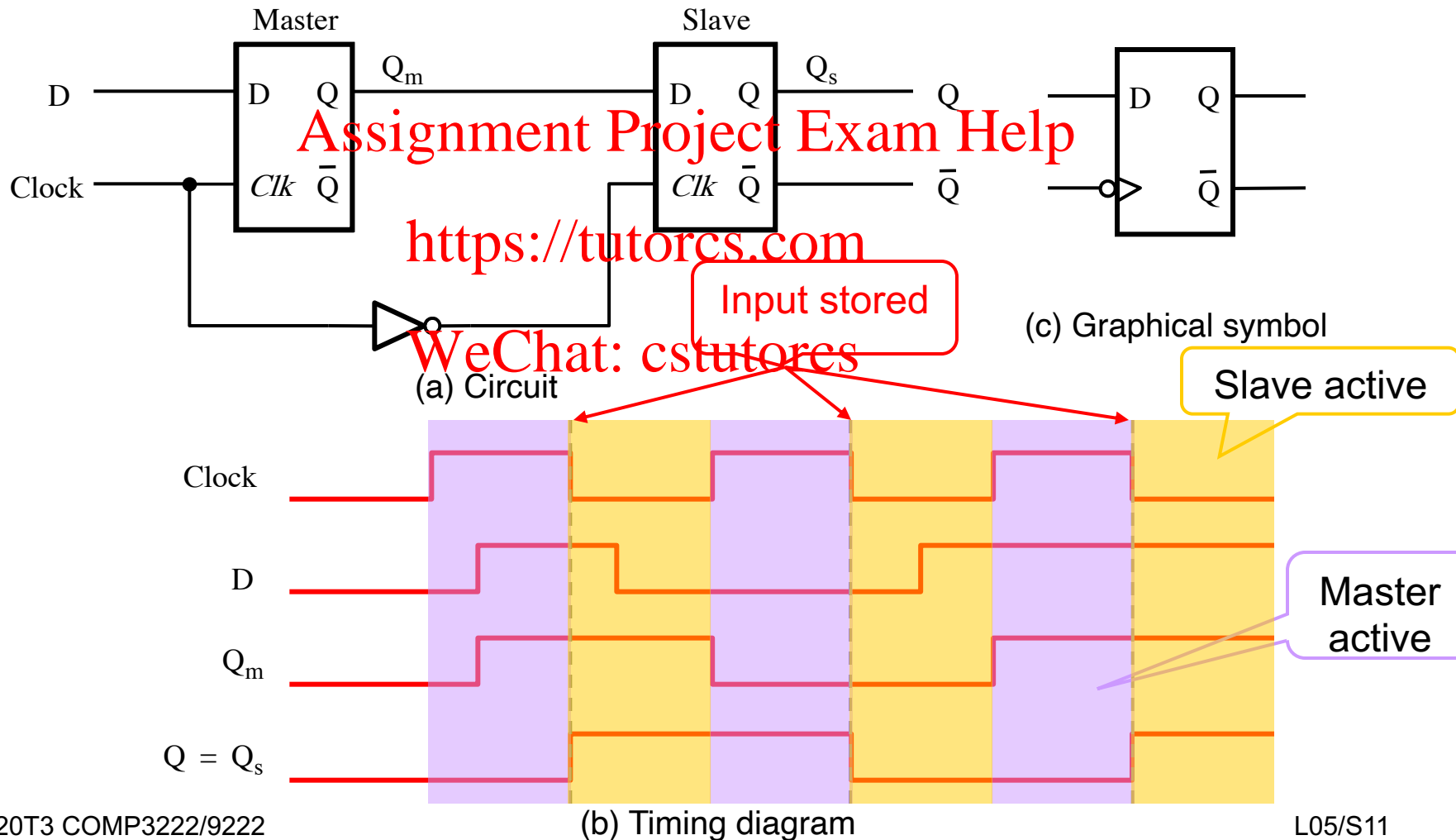
# Negative edge-triggered (Master-slave) D flip-flop

Latches are triggered by the level of the control signal, flip-flops are triggered on control signal transitions



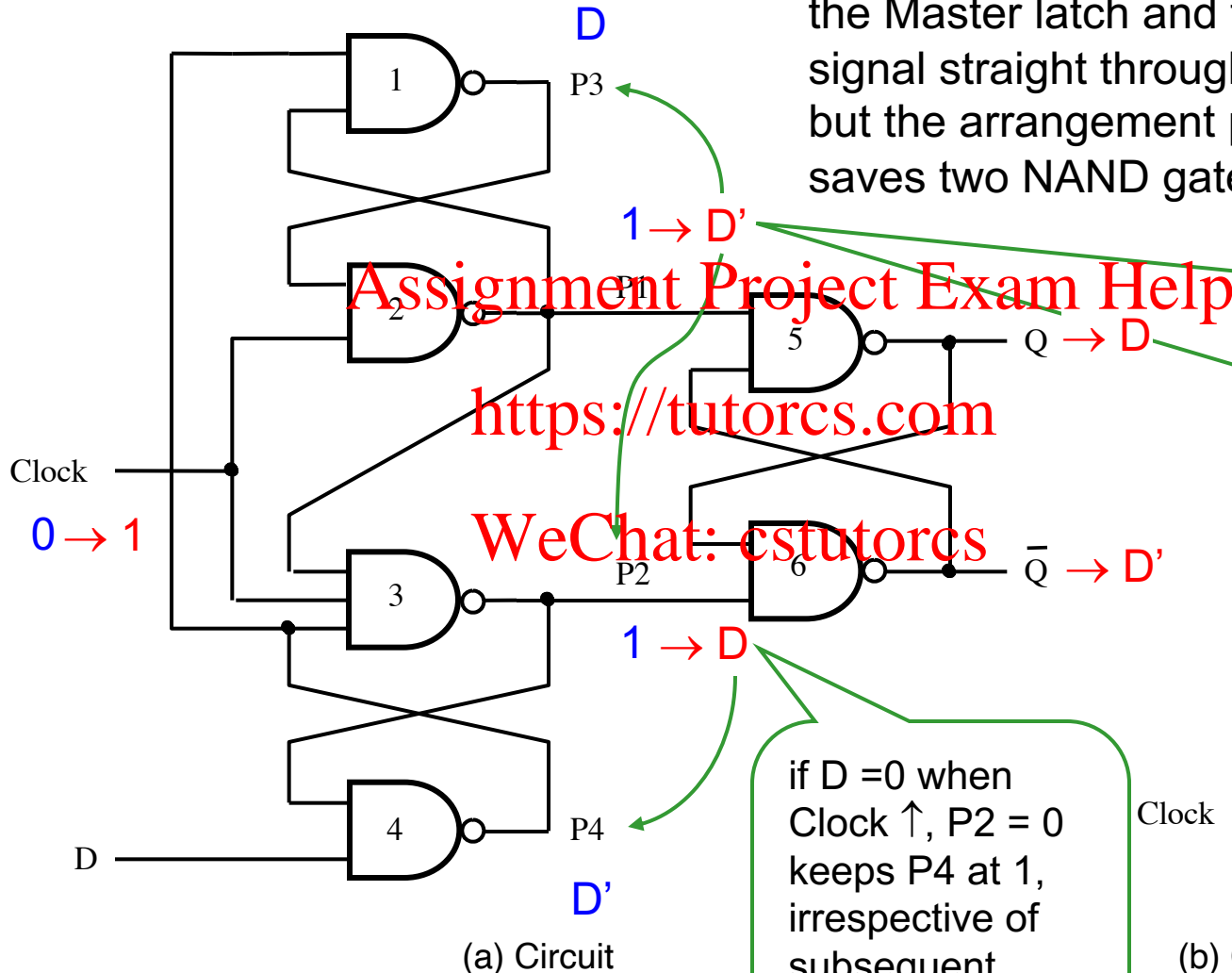
# A positive-edge-triggered D flip-flop

We could just invert the *Clk* input to the Master latch and feed the *Clk* signal straight through to the Slave, but the arrangement presented here saves two NAND gates and one inverter




if  $D = 1$  when  $\text{Clock} \uparrow$ ,  $P1 = 0$  keeps  $P2$  &  $P3$  at 1, irrespective of subsequent changes to  $D$  while Clock high

 if  $D = 0$  when  $\text{Clock} \uparrow$ ,  $P2 = 0$  keeps  $P4$  at 1, irrespective of subsequent changes to  $D$  while Clock high




(b) Graphical symbol
 
# Comparison of level-sensitive and edge-triggered D-type storage elements



(a) Circuit

 

(b) Timing diagram

# Recall the specification of implied memory

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY implied IS
```

```
    PORT ( A, B      : IN      STD_LOGIC ;
```

```
          AeqB       : OUT STD_LOGIC ) ;
```

```
END implied ;
```

```
ARCHITECTURE Behavior OF implied IS
```

```
BEGIN
```

```
    PROCESS ( A, B )
```

```
    BEGIN
```



```
        IF A = B THEN
```

```
            AeqB <= '1' ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

  

Resulting circuit has to remember the value of AeqB when A  $\neq$  B

# Code for a gated D latch

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, CLK : IN  STD_LOGIC ;
          Q : OUT  STD_LOGIC ) ;
END latch ;
```


Note: the PROCESS describing a latch, while exploiting *implicit memory*, complies with the *COMBINATIONAL* design rule that all signals that can affect the output are listed in the sensitivity list

<https://tutorcs.com>

```
ARCHITECTURE Behavior OF latch IS
```

```
BEGIN
    PROCESS ( D, CLK )
    BEGIN
        IF CLK = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

WeChat: cstutorcs

 

# Code for a positive edge-triggered D flip-flop


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, CLK : IN  STD_LOGIC ;
          Q : OUT STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( CLK )
    BEGIN
        IF CLK'event AND CLK = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

The signal attribute *'event'* is true when the signal transitions from one level to another

 Notes: (i) *SYNCHRONOUS PROCESSES* only list the clock signal in the sensitivity list; (ii) All assignment statements within a synchronous process should be guarded by a (*CLK'event AND CLK='1'*) condition; (iii) Each signal on the LHS of an assignment statement guarded by a (*CLK'event AND CLK='1'*) condition is the output of a flip-flop





# Equivalent code using a WAIT UNTIL statement

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY flipflop IS  
    PORT ( D, Clock : IN STD_LOGIC ;  
          Q : OUT STD_LOGIC ;  
END flipflop ;
```

```
ARCHITECTURE Behavior OF flipflop IS  
BEGIN
```

```
    PROCESS  
    BEGIN
```

```
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
```

```
        Q <= D ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

When used for the synthesis of a synchronous circuit, the WAIT UNTIL statement must be the first in a PROCESS block; all assignment statements that follow infer a flip-flop

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs


# Master-slave D flip-flop with *Clear* and *Preset*

- A design may call for a preset value on a FF
- Active low *Preset'* and *Clear'* inputs allow the flip-flop to be set to a given value asynchronously (independently of the *Clock*) – only one of them should be pulled low at a time

Assignment Project Exam Help

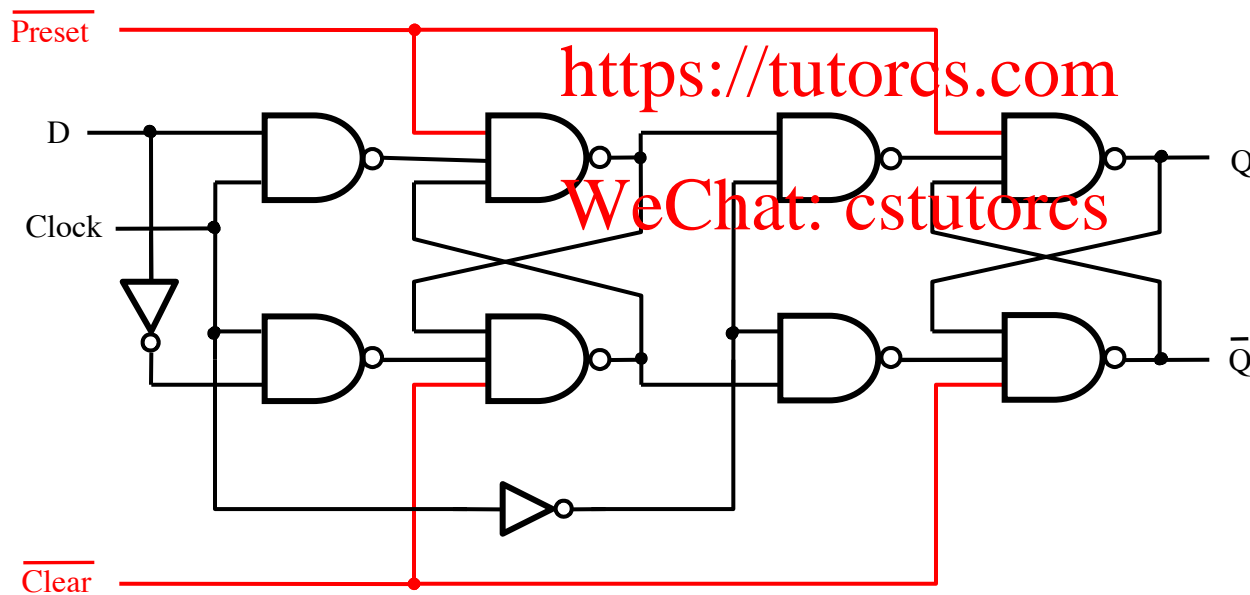


(a) Circuit

 

(b) Graphical symbol

- How long does the FF stay in the Clear or Preset state?

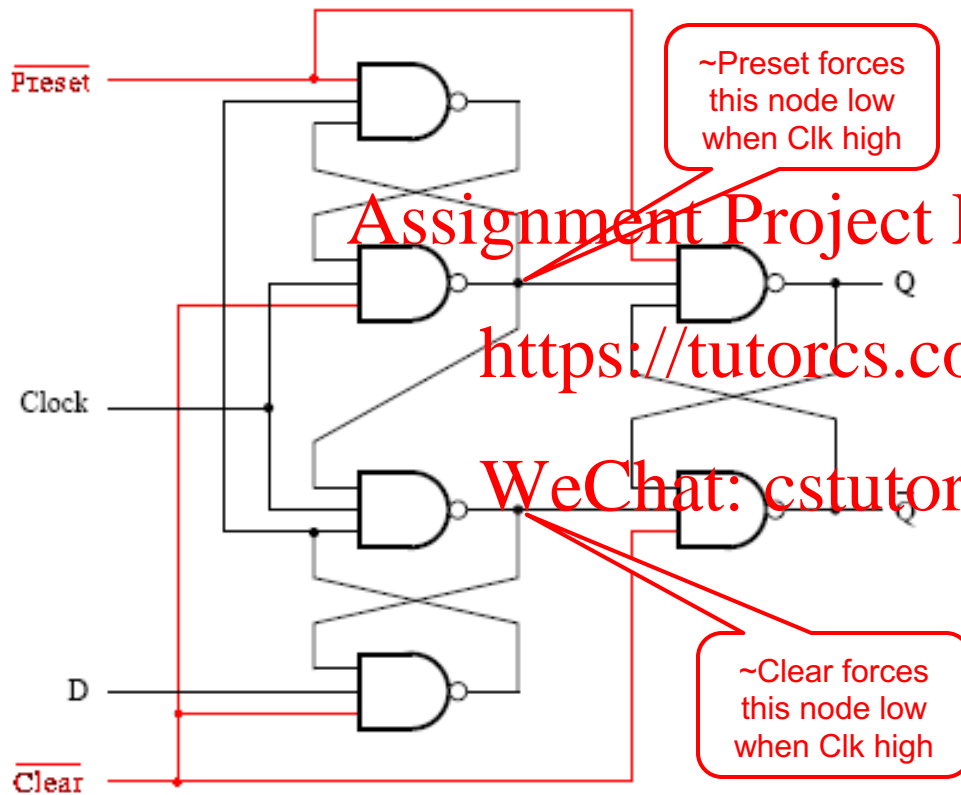
# Positive-edge-triggered D flip-flop with *Clear* and *Preset*



Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

 

(b) Graphical symbol

(a) Circuit

## Positive-edge-triggered D flip-flop with synchronous *Clear* and *Preset*

- Synchronous clear and preset is best done by gating the *D* input



Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

# D flip-flop with asynchronous reset

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY flipflop IS
```

```
    PORT ( D, Resetn, CLK : IN      STD_LOGIC ;
```

```
          Q               : OUT     STD_LOGIC) ;
```

```
END flipflop ;
```

```
ARCHITECTURE Behavior OF flipflop IS
```

```
BEGIN
```

```
    PROCESS ( Resetn, CLK)
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            Q <= '0' ;
```

```
        ELSIF CLK'EVENT AND CLK = '1' THEN
```

```
            Q <= D ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

Assignment Project Exam Help

<https://tutorcs.com>

WhatsApp: cstutorcs

Notes: (i) For a *synchronous process with an asynchronous reset/set*, both the CLK and the reset/set signal must be in the sensitivity list.

(ii) Only assign a constant, e.g. '0'/'1', to the FF output within the reset/set condition.

# D flip-flop with synchronous reset

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY flipflop IS
```

```
    PORT ( D, Resetn, Clock : IN      STD_LOGIC ;
```

```
          Q : OUT   STD_LOGIC) ;
```

```
END flipflop ;
```

```
ARCHITECTURE Behavior OF flipflop IS
```

```
BEGIN
```

```
    PROCESS
```

```
    BEGIN
```

```
        WAIT UNTIL Clock'EVENT AND Clock = '1';
```

```
        IF Resetn = '0' THEN
```

```
            Q <= '0' ;
```

```
        ELSE
```

```
            Q <= D ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Question: How do you specify this behaviour  
using an IF statement?

# Code for an **eight-bit register** with asynchronous reset

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY reg8 IS  
    PORT ( D          : IN      STD_LOGIC_VECTOR(7 DOWNTO 0) ;  
          Resetn, Clock : IN      STD_LOGIC ;  
          Q            : OUT     STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;  
END reg8;
```

<https://tutorcs.com>

```
ARCHITECTURE Behavior OF reg8 IS  
BEGIN  
    PROCESS (Resetn, Clock )  
    BEGIN  
        IF Resetn = '0' THEN  
            Q <= "00000000" ;  
        ELSIF Clock'EVENT AND Clock = '1' THEN  
            Q <= D ;  
        END IF ;  
    END PROCESS ;  
END Behavior ;
```

WeChat: cstutorcs

# Code for an *n*-bit register with asynchronous clear

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

Parameterized component with default value of 16 for the data width parameter N

```
ENTITY regn IS
```

```
    GENERIC ( N : INTEGER := 16 );
```

```
    PORT ( D      : IN      STD_LOGIC_VECTOR(N-1 DOWNTO 0);  
          Resetn, Clock : IN      STD_LOGIC;  
          Q      : OUT     STD_LOGIC_VECTOR(N-1 DOWNTO 0) );
```

```
END regn;
```

```
ARCHITECTURE Behavior OF regn IS  
BEGIN
```

```
    PROCESS (Resetn, Clock )
```

```
    BEGIN
```

```
        IF Resetn = '0' THEN
```

```
            Q <= (OTHERS => '0');
```

```
        ELSIF Clock'EVENT AND Clock = '1' THEN
```

```
            Q <= D ;
```

```
        END IF ;
```

```
    END PROCESS ;
```

```
END Behavior ;
```

Idiom for setting all bits of a signal to 0s

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs



# 8-bit register based on *regn* component

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY reg8 IS  
    PORT ( D          : IN      STD_LOGIC_VECTOR(7 DOWNTO 0) ;  
          Resetn, Clk : IN      STD_LOGIC ;  
          Q           : OUT     STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;  
END reg8 ;
```

```
ARCHITECTURE Structure OF reg8 IS
```

```
BEGIN
```

```
    reg8: regn
```

```
        GENERIC MAP ( N => 8 )
```

```
        PORT MAP ( D, Resetn, Clk, Q);
```

```
END Structure ;
```


<https://tutorcs.com>

WeChat: cstutorcs

Assumes *regn* component  
declared in the working  
directory

GENERIC MAP used to  
overwrite default parameter  
value

# A simple shift register

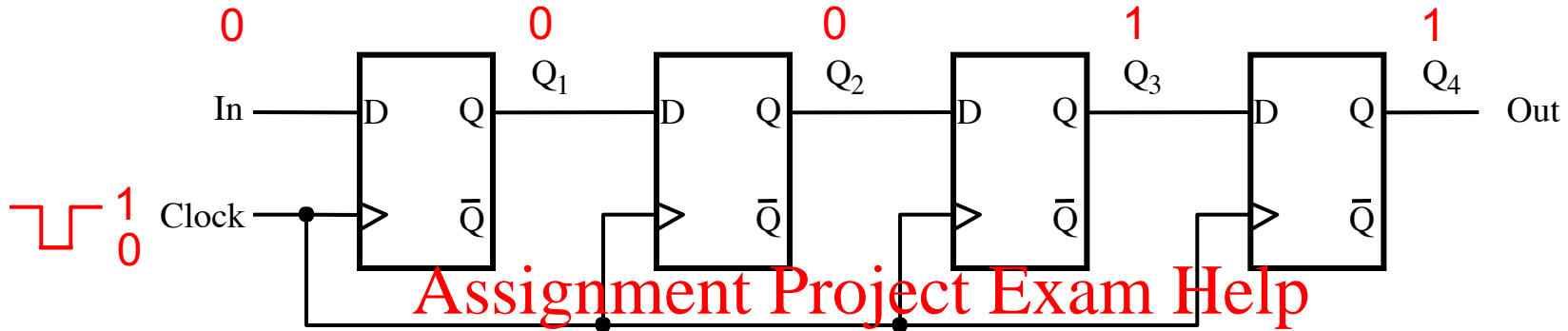


<https://tutorcs.com>

WeChat: cstutorcs

	In	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>	Q <sub>4</sub> = Out
$t_0$	1	0	0	0	0
$t_1$	0	1	0	0	0
$t_2$	1	0	1	0	0
$t_3$	1	1	0	1	0
$t_4$	1	1	1	0	1
$t_5$	0	1	1	1	0
$t_6$	0	0	1	1	1
$t_7$	0	0	0	1	1

# Parallel-access shift register

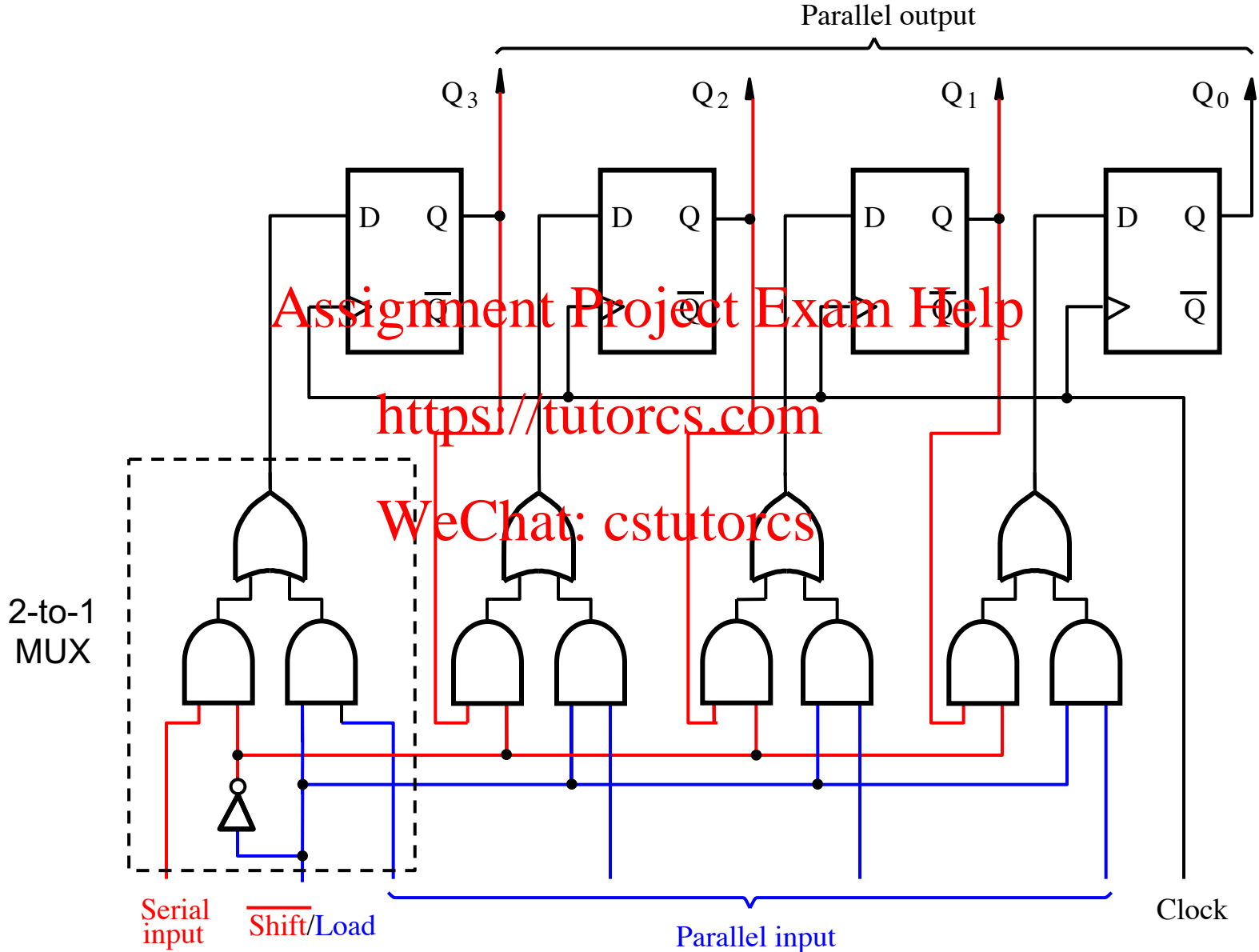

# Behavioural code for a D flip-flop with a 2-to-1 multiplexer on the *D* input

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

```
ENTITY muxdff IS
    PORT ( D0, D1, Sel, Clock : IN      STD_LOGIC ;
           Q                   : OUT    STD_LOGIC ) ;
END muxdff;
```

```
ARCHITECTURE Behavior OF muxdff IS
BEGIN
```

```
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1';
        IF Sel = '0' THEN
            Q <= D0 ;
        ELSE
            Q <= D1 ;
        END IF ;
    END PROCESS ;
```

```
END Behavior ;
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

-- or:

```
-- PROCESS (Clock)
-- BEGIN
--     IF Clock' ... THEN
--         IF Sel ...
--             etc.
--     END IF;
-- END IF;
```

# Hierarchical code for a four-bit shift register

- Design hierarchies are recursive *structures* comprised of components, or sub-circuits, whose architectures, at the leaf level, are expressed in terms of their behaviours


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
```

BUFFER mode allows Q to be used in both IN and OUT modes

```
ENTITY shift4 IS
  PORT ( P      : IN  STD_LOGIC_VECTOR( 3 DOWNT0 0) ;
        ser, ld, Clock : IN  STD_LOGIC ;
        Q      : BUFFER STD_LOGIC_VECTOR( 3 DOWNT0 0) ) ;
END shift4;
```

```
ARCHITECTURE Structure OF shift4 IS
  COMPONENT muxdff
    PORT ( D0, D1, Sel, Clock : IN  STD_LOGIC ;
          Q      : OUT STD_LOGIC ) ;
  END COMPONENT;
BEGIN
  Stage3: muxdff PORT MAP ( ser, P(3), ld, Clock, Q(3) );
  Stage2: muxdff PORT MAP ( Q(3), P(2), ld, Clock, Q(2) );
  Stage1: muxdff PORT MAP ( Q(2), P(1), ld, Clock, Q(1) );
  Stage0: muxdff PORT MAP ( Q(1), P(0), ld, Clock, Q(0) );
END Structure ;
```

Flip-flops

 

# Alternative (behavioural) code for a shift register

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY shift4 IS
4      PORT ( P          : IN          STD_LOGIC_VECTOR( 3 DOWNT0 0) ;
5             ser, ld, Clock : IN          STD_LOGIC ;
6             Q          : BUFFER      STD_LOGIC_VECTOR( 3 DOWNT0 0) ) ;
7  END shift4;

8  ARCHITECTURE Behavior OF shift4 IS
9  BEGIN
10     PROCESS
11     BEGIN
12         WAIT UNTIL Clock'EVENT AND Clock = '1' ;
13         IF ld = '1' THEN
14             Q <= P ;
15         ELSE
16             Q(0) <= Q(1) ;
17             Q(1) <= Q(2) ;
18             Q(2) <= Q(3) ;
19             Q(3) <= ser ;
20         END IF ;
21     END PROCESS ;
22 END Behavior ;
```

**Assignment Project Exam Help**  
<https://tutorcs.com>  
**WeChat: cstutorcs**

**BUFFER mode allows Q to appear on both the left and right sides of signal assignments**

**A WAIT UNTIL statement implies all signals assigned a value inside the process are implemented as the output of a flip-flop**

Flip-flops

L05/S30

# Identical code, which reverses the ordering of statements 16 – 19 in L05/S30

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY shift4 IS
4      PORT ( P          : IN          STD_LOGIC_VECTOR( 3 DOWNT0 0) ;
5              ser, Id, Clock : IN          STD_LOGIC ;
6              Q          : BUFFER     STD_LOGIC_VECTOR( 3 DOWNT0 0) ) ;
7  END shift4;

8  ARCHITECTURE Behavior OF shift4 IS
9  BEGIN
10     PROCESS
11     BEGIN
12         WAIT UNTIL Clock'EVENT AND Clock = '1' ;
13         IF Id = '1' THEN
14             Q <= P ;
15         ELSE
16             Q(3) <= ser ;
17             Q(2) <= Q(3) ;
18             Q(1) <= Q(2) ;
19             Q(0) <= Q(1) ;
20         END IF ;
21     END PROCESS ;
22 END Behavior ;
```

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

IMPORTANT:

Why is the statement order immaterial?

# Code for an $n$ -bit left-to-right shift register

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all ;

3  ENTITY shiftn IS
4      GENERIC ( N : INTEGER := 8 ) ;
5      PORT ( P      : IN      STD_LOGIC_VECTOR( N-1 DOWNT0 0 ) ;
6            ser, Id, Clock : IN      STD_LOGIC ;
7            Q      : BUFFER STD_LOGIC_VECTOR( N-1 DOWNT0 0 ) ) ;
8  END shiftn;
```

```
9  ARCHITECTURE Behavior OF shiftn IS
10 BEGIN
11     PROCESS
12     BEGIN
13         WAIT UNTIL Clock EVENT AND Clock = '1';
14         IF Id = '1' THEN
15             Q <= P ;
16         ELSE
17             Genbits: FOR i IN 0 to N-2 LOOP
18                 Q(i) <= Q(i+1) ;
19             END LOOP ;
20             Q(N-1) <= ser ;
21         END IF ;
22     END PROCESS ;
23 END Behavior ;
```

Just as the FOR...GENERATE statement is used to generate a set of concurrent statements, the FOR...LOOP statement is used to generate a set of sequential statements



# Flip-flop timing parameters

Three important parameters that need to be considered in the design of sequential circuits:


- *Propagation delay*,  $t_{cQ}$ , the time needed for the output of the FF to change after the triggering clock edge has occurred
- *Setup time*,  $t_{su}$ , the time interval the input needs to be stable for prior to the triggering clock edge, for it to be reliably read
- *Hold time*,  $t_h$ , the time interval the input needs to be stable for after the triggering clock edge, for it to be reliably read

WeChat: cstutorcs


- The magnitude of these parameters depend upon the design of the flip-flop, the process technology used to implement them, and the source voltage
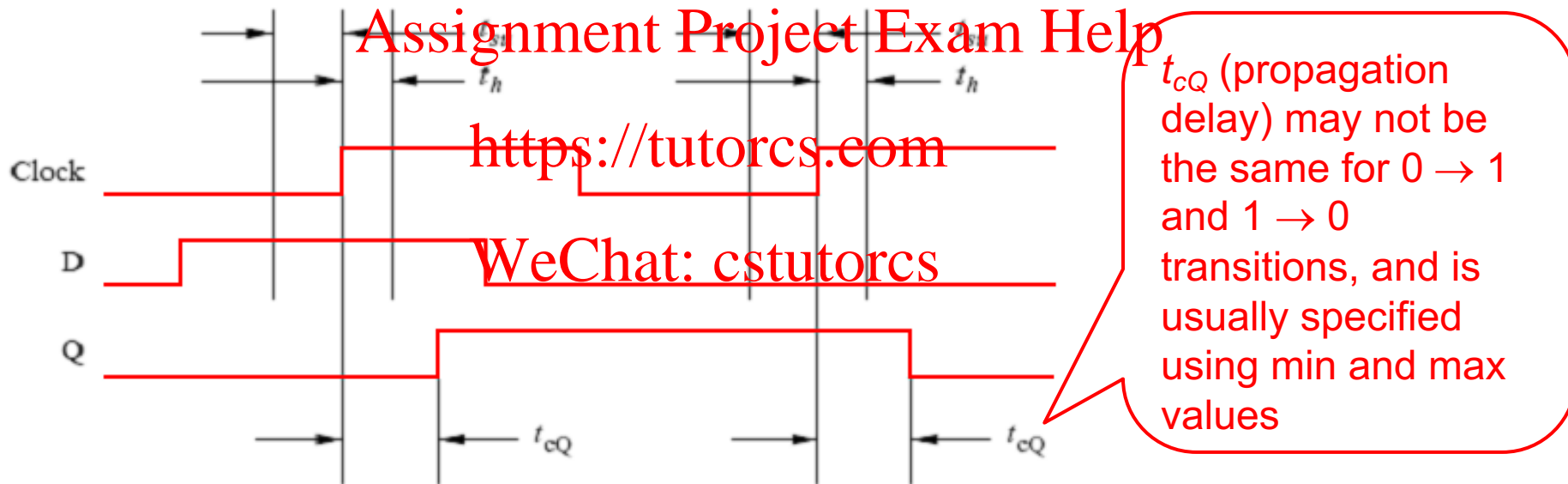
# Propagation delay

*Propagation delay is the time it takes for the new value to emerge from a flip-flop after the triggering edge*



# $t_{cQ}$ for a gated D latch

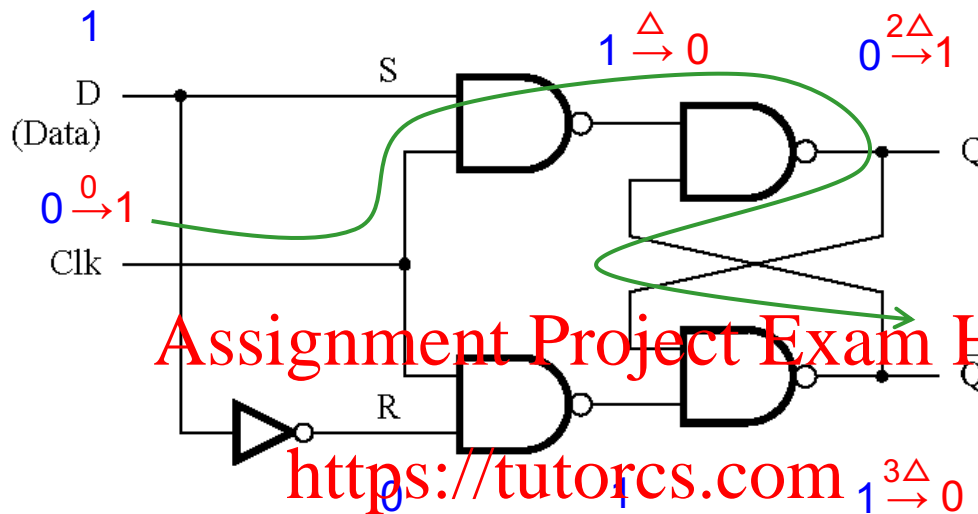


Assignment Project Exam Help

<https://tutorcs.com>

Here,  $t_{cQ}$  is  $2\Delta$  for 0 $\rightarrow$ 1 transitions, but  $3\Delta$  for 1 $\rightarrow$ 0 transitions


WeChat: cstutorcs

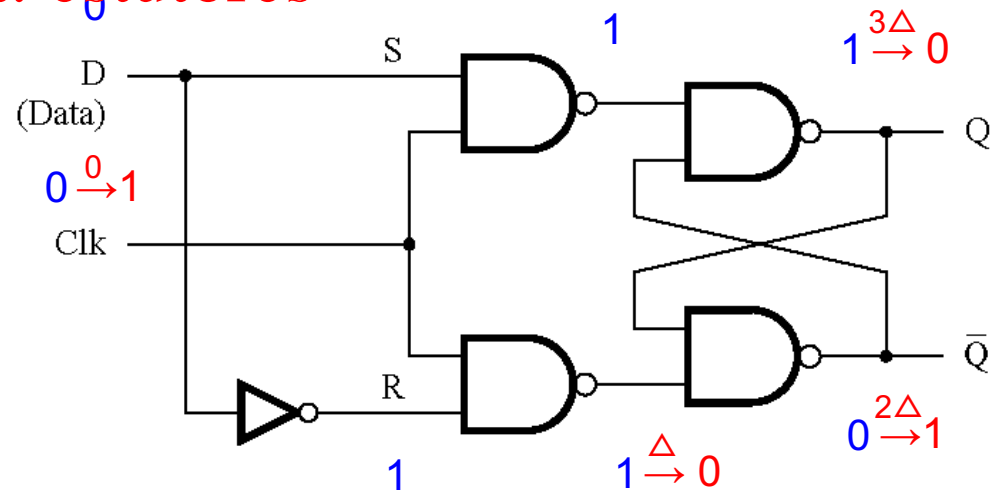
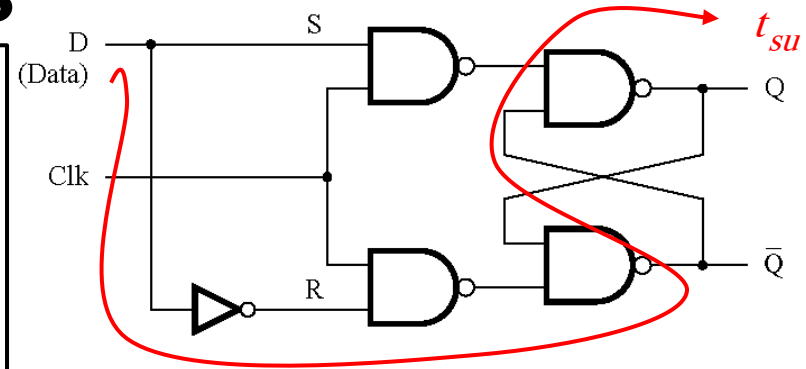
# Setup and hold times

The designer of the circuit that generates the  $D$  signal must ensure setup and hold times are satisfied

Together, they define a window of time around the triggering clock edge during which  $D$  must be stable



(a) Circuit

Assignment Project Exam Help


$t_{su} \Rightarrow$  a change in  $D$  has to have had time to be seen at the outputs before the negative Clk edge

<https://tutorcs.com>


- Typical values for 28nm CMOS

are  $t_{su} = 0.03 \text{ ns}$  and  $t_h = 0.02 \text{ ns}$


WeChat: cstutorcs

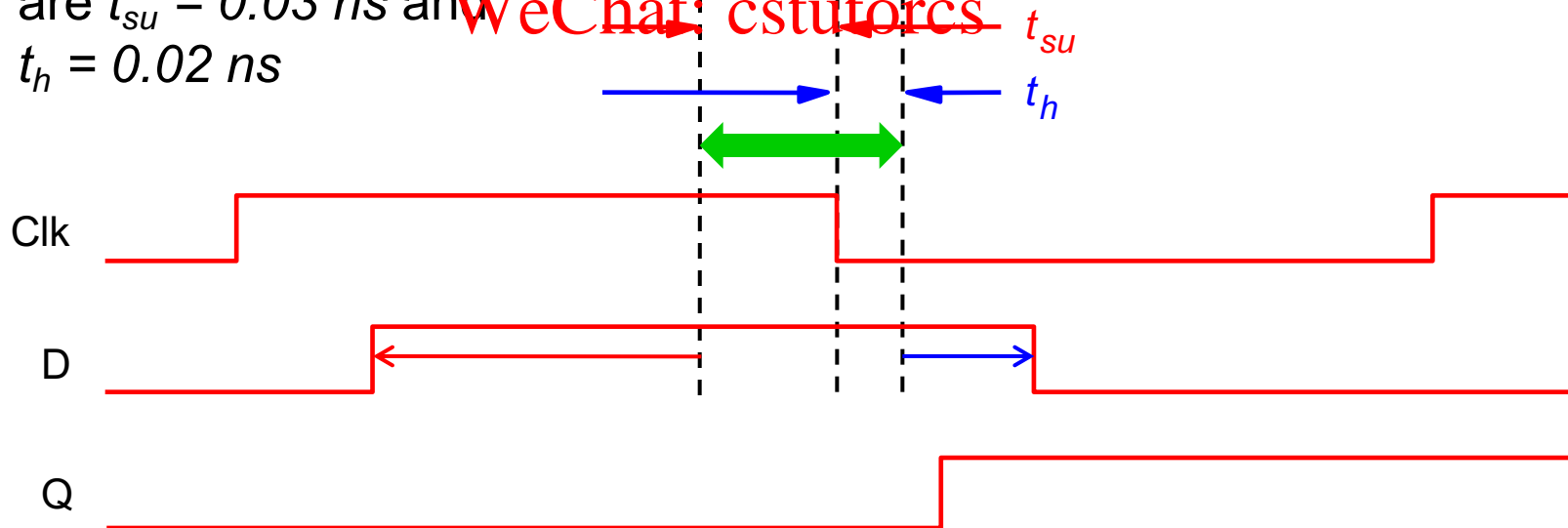
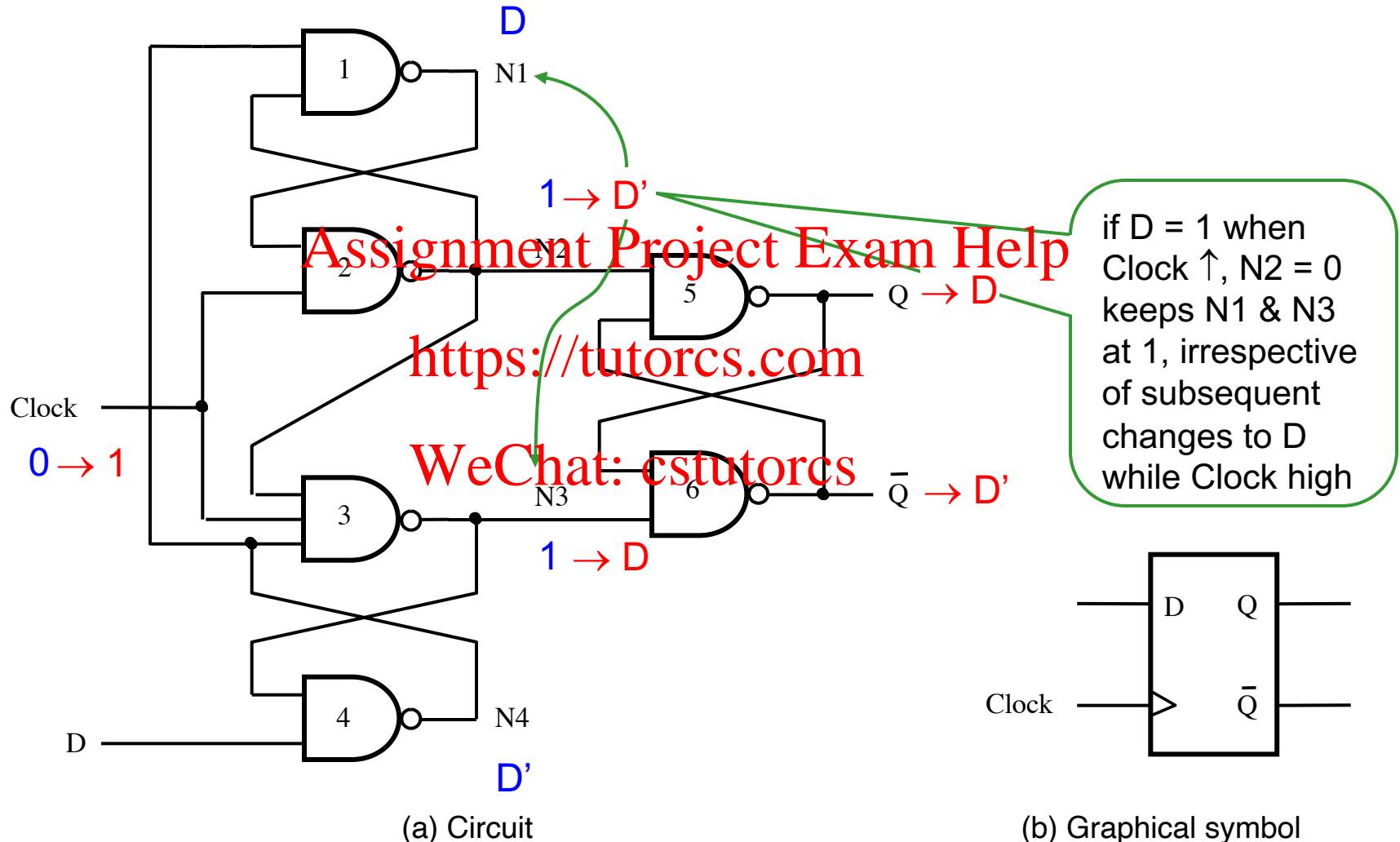
# Recall positive-edge-triggered D flip-flop



 
# $t_h$ for a positive-edge-triggered D flip-flop




Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

 


(a) Normal operation

 


(b) Hold time violation

The larger  $\varepsilon$  is, the less likely it is for N2 to be held high

# T flip-flop

 

(a) Circuit

 


(b) Graphical symbol

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

(d) Characteristic table

$$Q(t+1) = T \cdot Q'(t) + T' \cdot Q(t) \\ = T \text{ XOR } Q(t)$$



(e) Characteristic equation:

 

(c) Timing diagram
 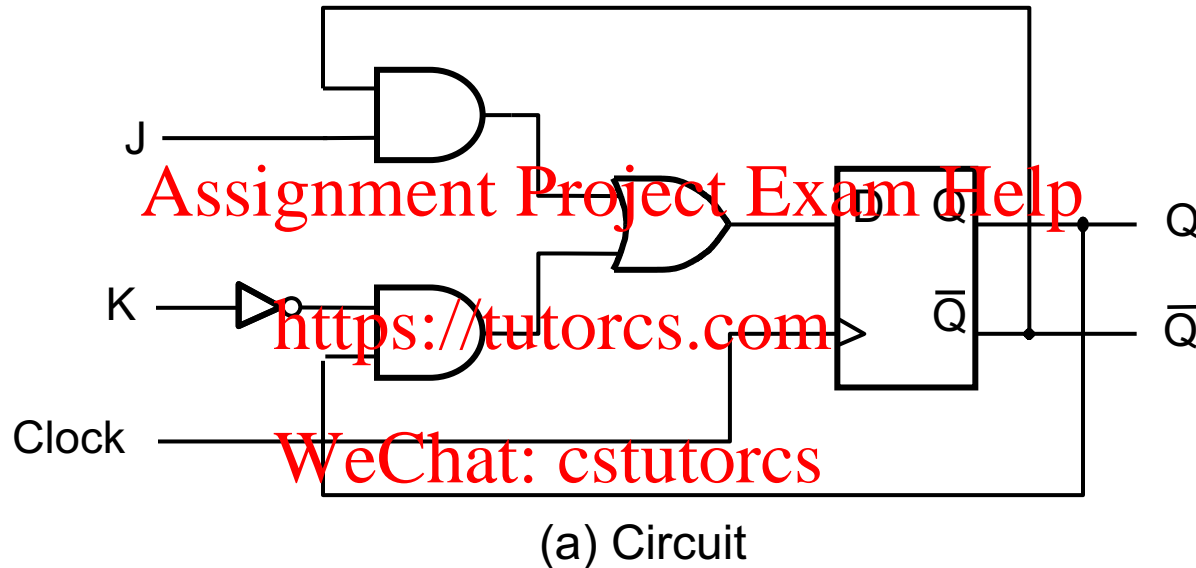
# JK flip-flop

- Combines the features of an SR flip-flop and a T flip-flop



(b) Graphical symbol

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$


(c) Characteristic table



# A three-bit up-counter (ripple counter)


T	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q}(t)$

Characteristic table

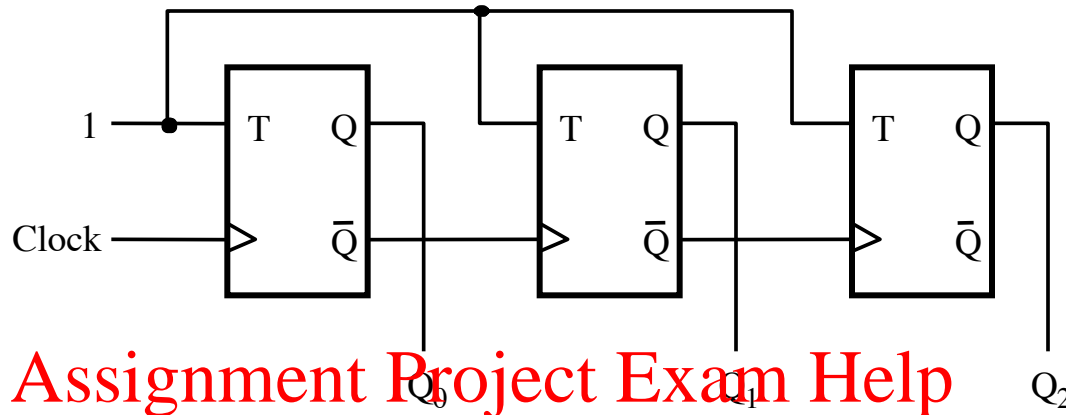


Assignment Project Exam Help

 The ripple effect of the triggering edge due to  $t_{cQ}$  propagation delays causes glitching from 011  $\rightarrow$  010  $\rightarrow$  000  $\rightarrow$  100




# A three-bit down-counter

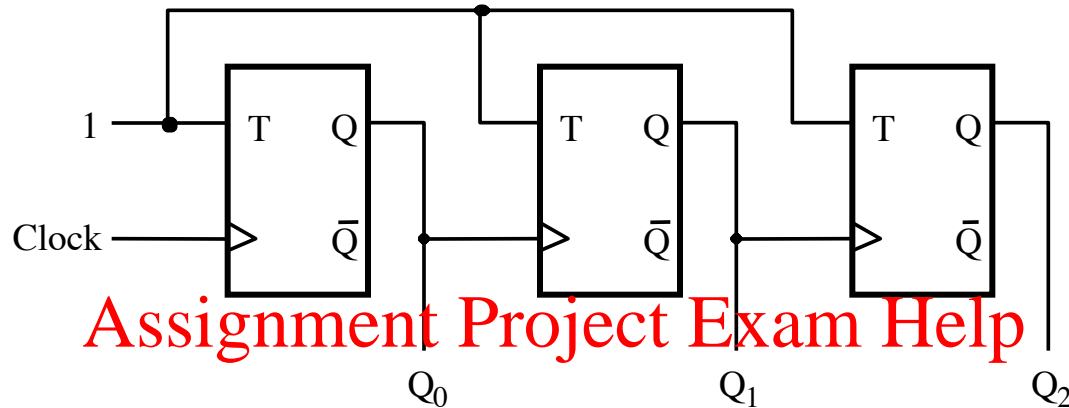

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

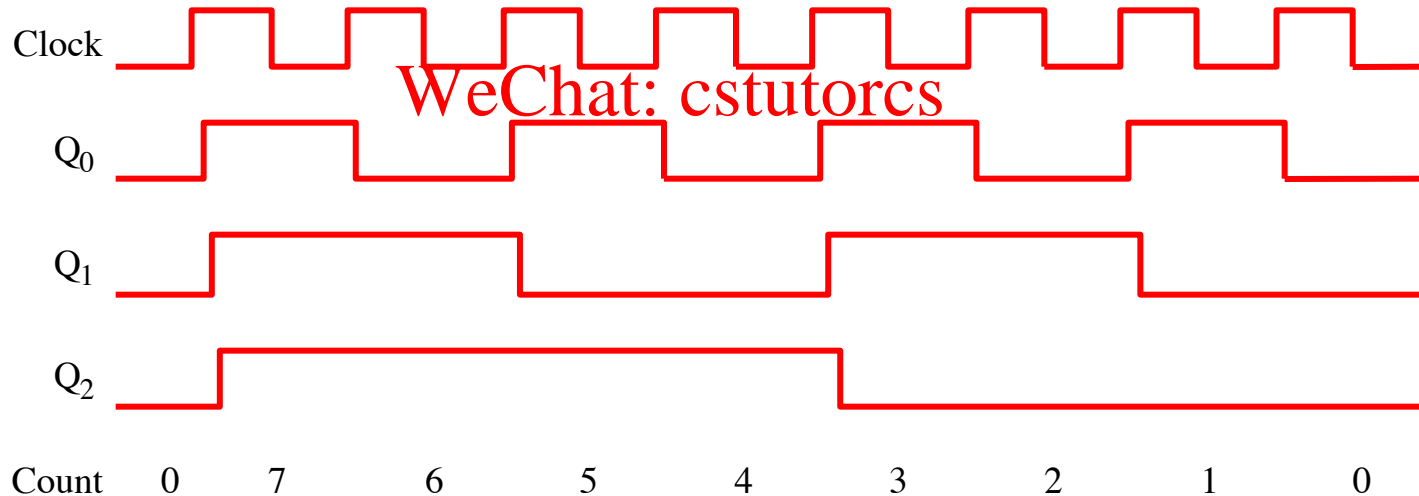

Timing diagram

# Derivation of a synchronous up-counter

In which all output bits change at the same time

- based on T flip-flops triggered by the one clock signal

Clock cycle	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0



Assignment Project Exam Help  
<https://tutorcs.com>  
 WeChat: cstutorcs

Q<sub>1</sub> changes  
 Q<sub>2</sub> changes

$T_0 = 1$   
 $T_1 = Q_0$   
 $T_2 = Q_0Q_1$   
 $T_3 = Q_0Q_1Q_2$   
 $\dots$   
 $T_n = Q_0Q_1\dots Q_{n-1}$

 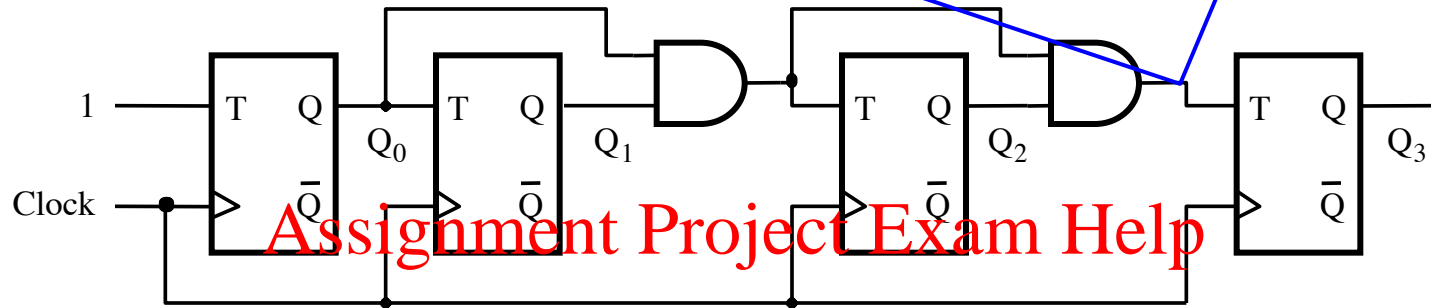
# A four-bit synchronous up-counter

Need to ensure that the  $clock\_period \geq t_{cQ} + \text{delay of the AND gate chain} + t_{su}$





## Timing diagram
 
# Inclusion of an Enable and asynchronous Clear capability


 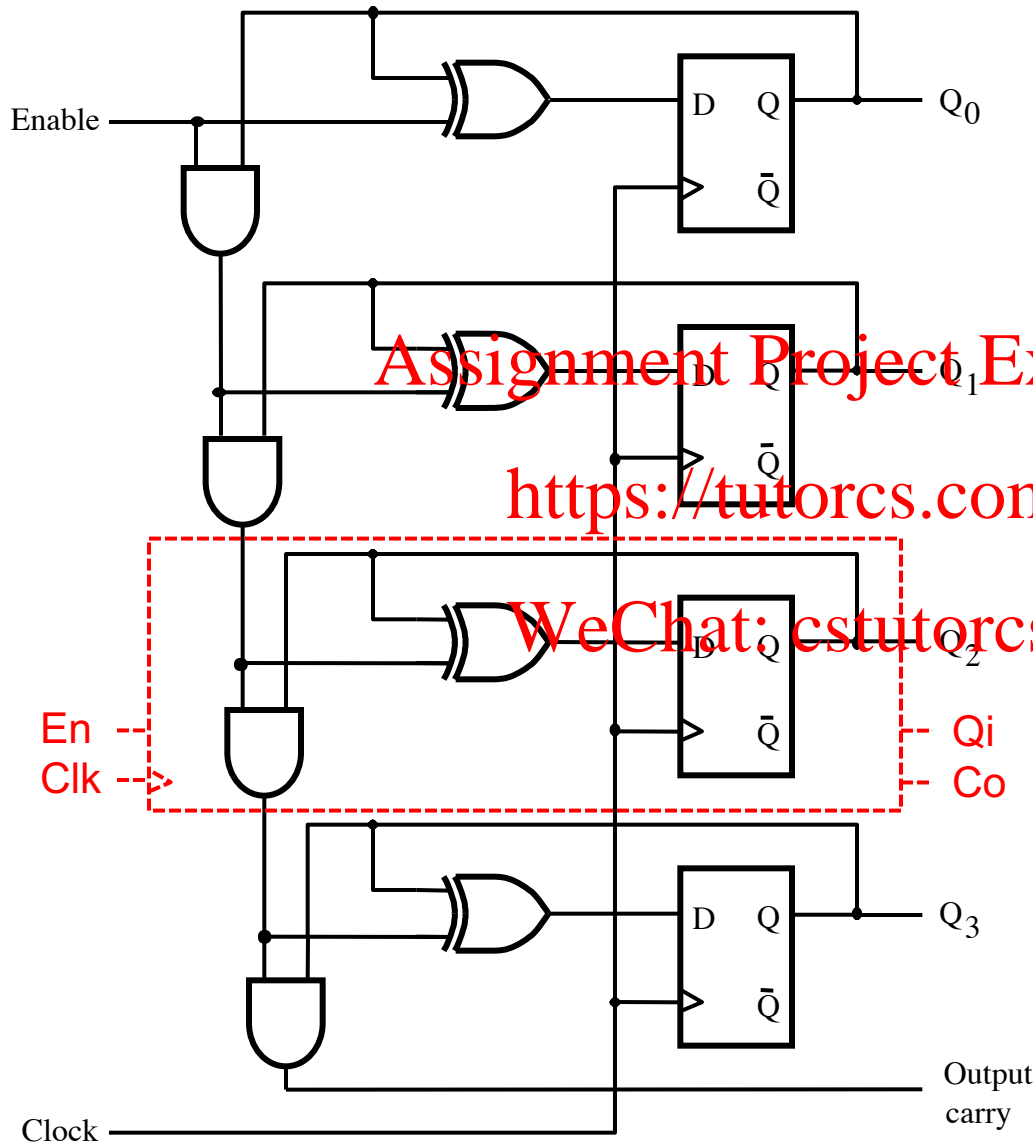
# A four-bit synchronous counter with D FFs



T flip-flop:  
 $Q(t+1) = T \text{ XOR } Q(t)$

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

Can you see how you would describe the structure in VHDL?

# Behavioural code for a four-bit up-counter with asynchronous clear

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.std_logic_unsigned.all ;
```

Needed to be able  
to increment Count

```
ENTITY upcount IS  
    PORT ( Clock, Resetn, E : IN          STD_LOGIC ;  
           Q : OUT          STD_LOGIC_VECTOR(3 DOWNTO 0) );  
END upcount;
```

Assignment Project Exam Help

```
ARCHITECTURE Behavior OF upcount IS  
    SIGNAL Count : STD_LOGIC_VECTOR(3 DOWNTO 0);  
BEGIN
```

<https://tutorcs.com>

```
    PROCESS (Clock, Resetn)  
    BEGIN
```

WeChat: cstutorcs

Advantages of behavioural  
code over structural code for  
this design?


```
        IF Resetn = '0' THEN  
            Count <= "0000";  
        ELSIF (Clock'EVENT AND Clock = '1') THEN  
            IF E = '1' THEN  
                Count <= Count + 1 ;  
            ELSE  
                Count <= Count ;
```

While not required  
because of implied  
memory semantics,  
this statement is  
included for clarity

```
            END IF ;  
        END IF ;  
    END PROCESS ;  
    Q <= Count ;  
END Behavior ;
```
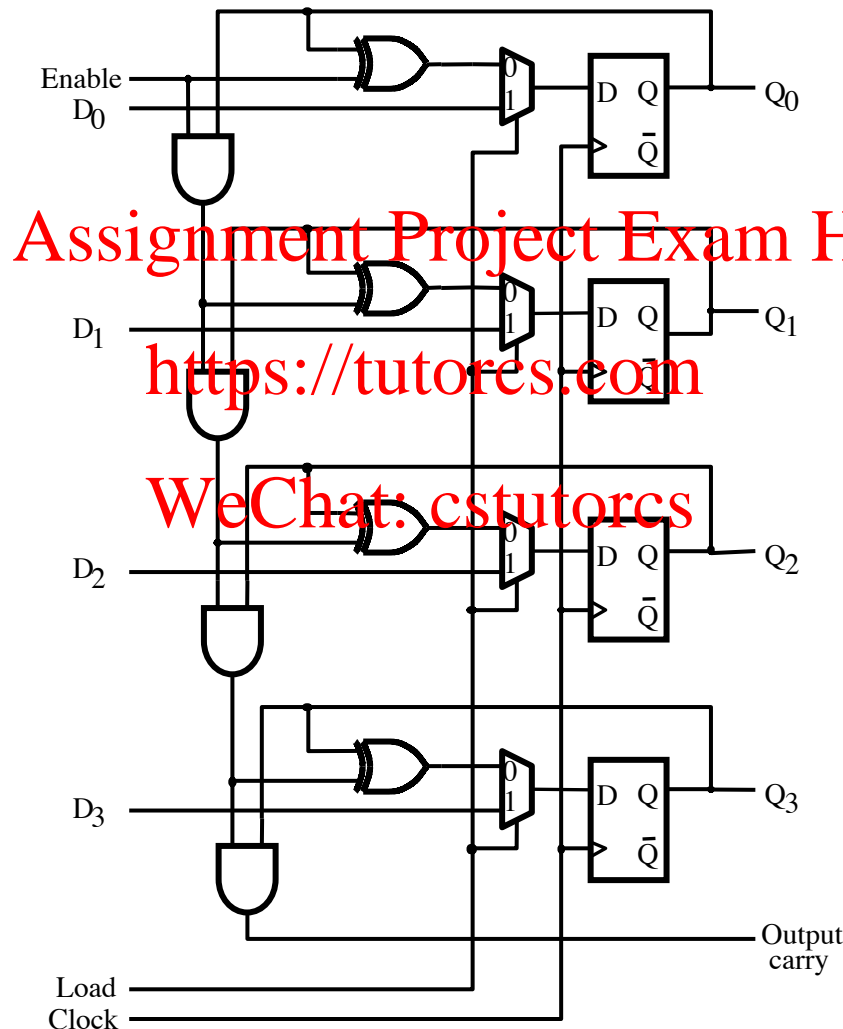
# Starting the count from any value

- A counter with parallel-load capability





# A four-bit counter with parallel load, using INTEGER signals

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY upcount IS
    PORT (
        R      : IN      INTEGER RANGE 0 TO 15 ;
        Clock, Resetn, L : IN      STD_LOGIC ;
        Q      : BUFFER  INTEGER RANGE 0 TO 15 );
END upcount;

ARCHITECTURE Behavior OF upcount IS
BEGIN
    PROCESS (Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Q <= 0 ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF L = '1' THEN
                Q <= R ;
            ELSE
                Q <= Q + 1 ;
            END IF;
        END IF ;
    END PROCESS ;
END Behavior ;
```


Assignment Project Exam Help

<https://tutorcs.com>



WeChat: cstutorcs
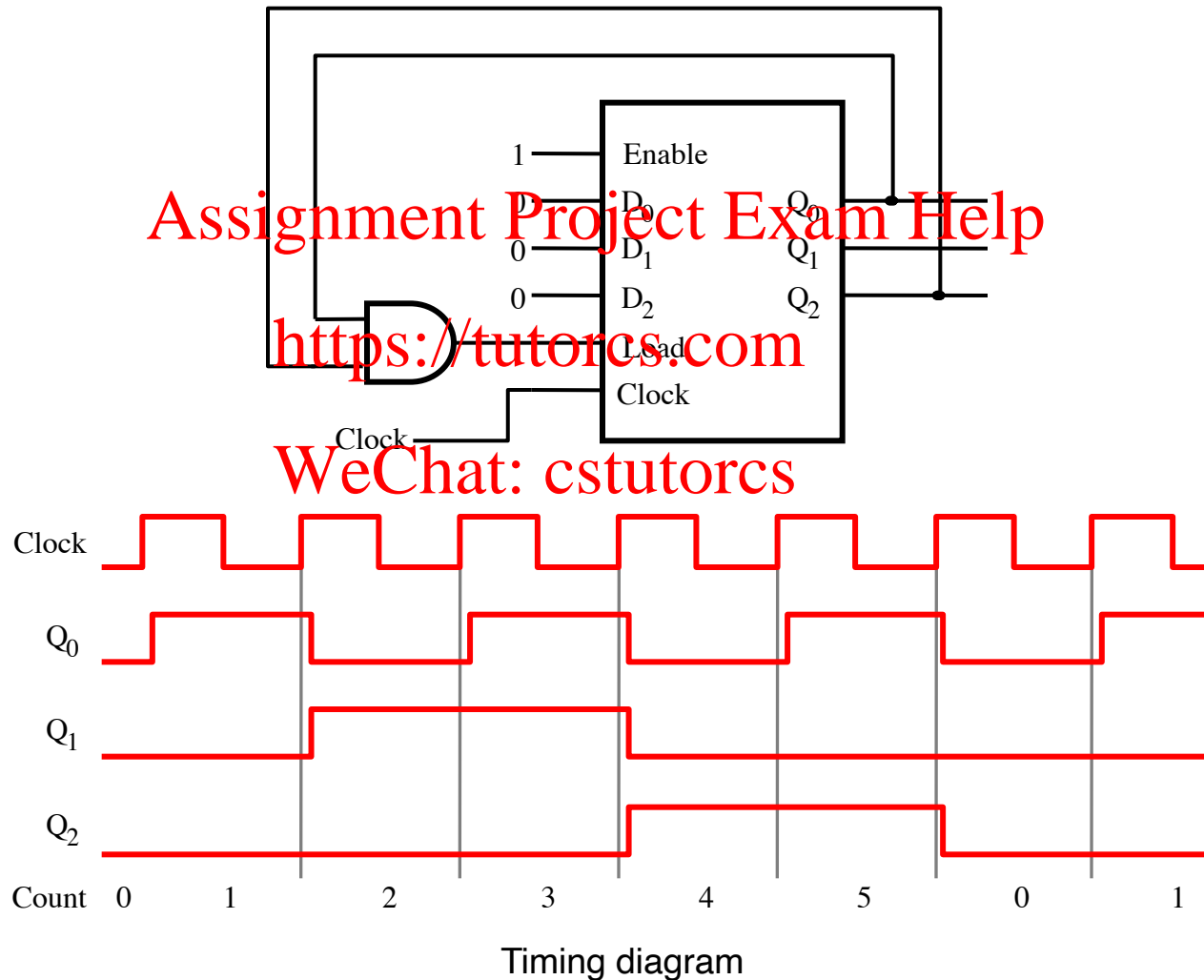
# Controlling the count range

- A modulo-6 counter with synchronous reset


 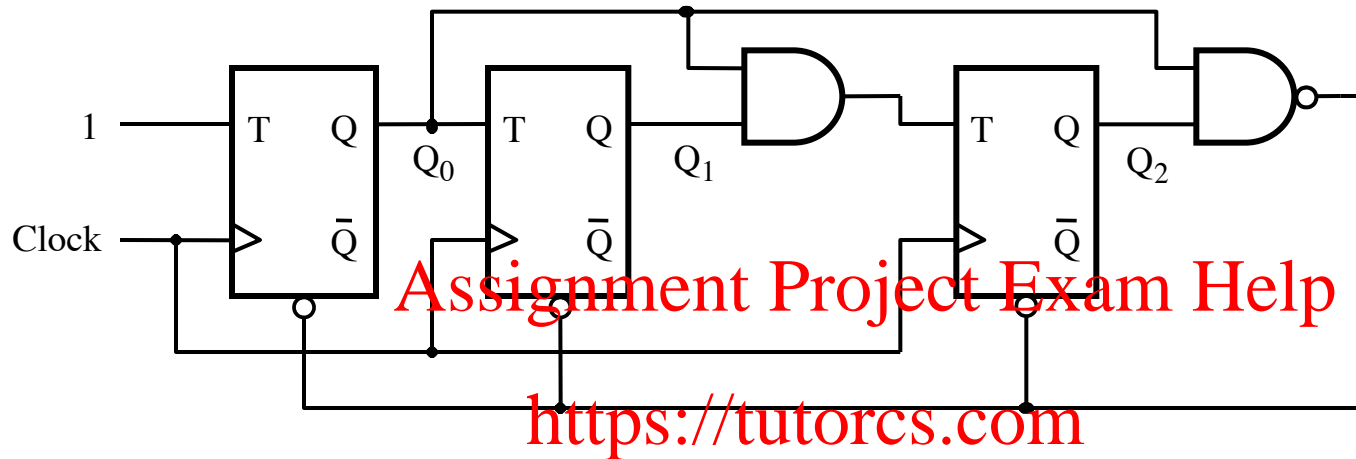
# A modulo-6 counter with asynchronous reset



Glitching is undesirable: can have unintended consequences if not designed away from the outset

# Code for a down-counter

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY downcnt IS
    GENERIC ( modulus          : INTEGER := 8 ) ;
    PORT (   Clock, L, E       : IN          STD_LOGIC ;
            Q                   : OUT        INTEGER RANGE 0 TO modulus-1 ) ;
END downcnt;


ARCHITECTURE Behavior OF downcnt IS
    SIGNAL Count : INTEGER RANGE 0 TO modulus-1 ;
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
        IF L = '1' THEN
            Count <= modulus-1 ;
        ELSE
            IF E = '1' THEN
                Count <= Count-1 ;
            END IF;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;
```

Assignment Project Exam Help


<https://tutorcs.com>

WeChat: cstutorcs


# A two-digit BCD counter

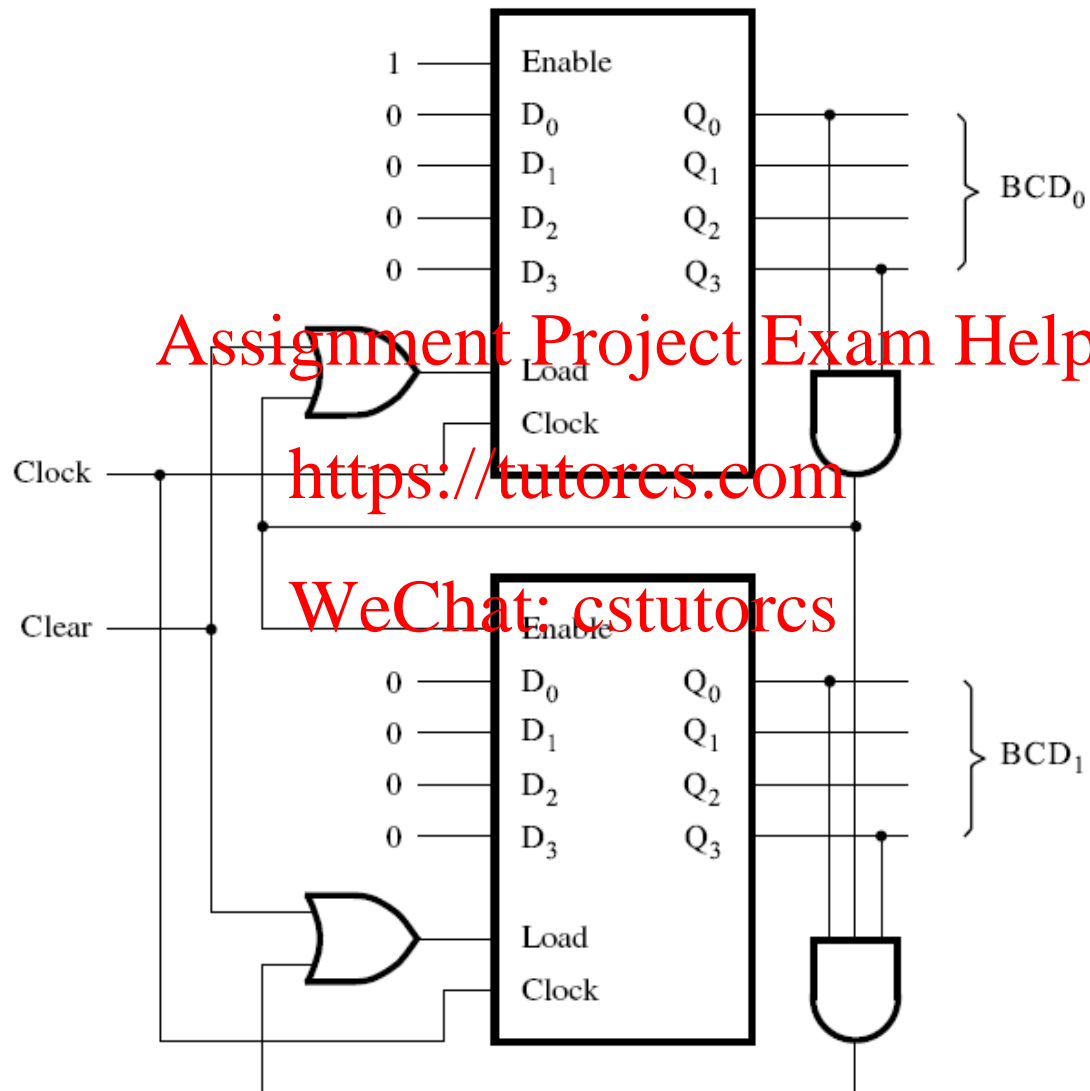

# Ring counter

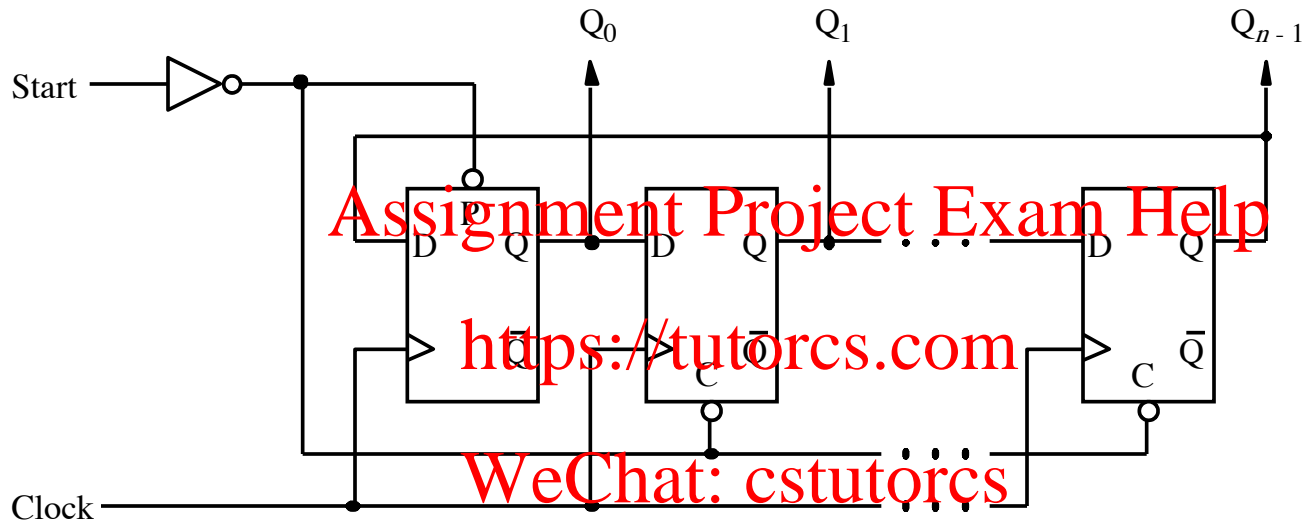

(a) An  $n$ -bit ring counter

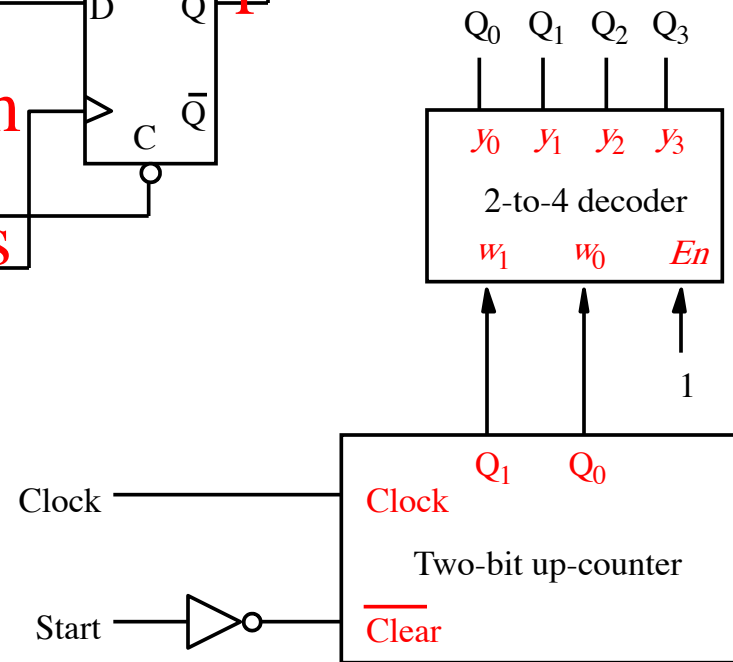

(b) A four-bit ring counter

# Timing analysis of flip-flop circuits

- Usually the maximum clock frequency a circuit can be operated at,  $F_{max}$ , needs to be determined
- Whether any hold times are violated also needs to be determined
- Timing parameters of flip-flops were introduced in slides L05/S33 to L05/S38 – these include the set-up time  $t_{su}$ , the hold time  $t_h$ , and the clock-to-Q propagation delay  $t_{cQ}$

<https://tutorcs.com>

WeChat: cstutorcs


# Timing analysis of a simple flip-flop circuit

- Consider the simple circuit shown, and let's assume that  $t_{su} = 0.6$  ns,  $t_h = 0.4$  ns, and  $0.8$  ns  $\leq t_{cQ} \leq 1.0$  ns
  - Furthermore, assume the delay of a  $k$ -input gate is  $1 + 0.1k$  ns
  - To calculate  $T_{min} = 1/F_{max}$ , we need to determine the longest timing path in the circuit (a.k.a. *critical path*) that starts and ends at a flip-flop
  - Here:
 

$$\min\{t_{cQ}\} + t_{NOT} = 0.8 + 1.1 = 1.9$$

$$> t_h = 0.4$$
 
$$\therefore \text{no violation}$$
  - Need to check hold time violations by considering the shortest possible delay from any +ve clock edge to any flip-flop input
- any faster, and  $t_{su}$  would not be satisfied





# Timing analysis of a 4-bit counter

Assume the same timing parameters as in the previous example; critical path:


$$T_{min} = \max\{t_{cQ(Q0)}\} + 3(t_{AND}) + t_{XOR} + t_{su(Q3)}$$

$$= 1.0 + 3(1.2) + 1.2 + 0.6$$

$$= 6.4 \text{ ns}$$

$F_{max} = 1/6.4 \text{ ns} = 156 \text{ MHz}$   
 (this assumes Enable is well behaved; if not,  $F_{max}$  may need to be reduced)

 
Shortest path from clock to D for each FF is  $\min\{t_{cQ}\} + t_{XOR} = 0.8 + 1.2 = 2.0 \text{ ns} > t_h = 0.4 \text{ ns} \therefore$   
 no hold violations (given Enable is well behaved)




Q: When is it best to (de)assert *Enable*?
 
# Clock skew


- Clock skew is the spread in time (relative delay) in clock edges arriving at the various synchronous components of a digital circuit
- Mostly, these are caused by wire delays
- FPGAs have special clock distribution networks, which use low-resistance (fat) wiring tracks, buffers that amplify the clock signal, and “balanced” layouts, such as H-trees with the root located at the centre of the chip, to minimize clock skew



# Effect of clock skew on $F_{max}$

 

 
- Assume  $t_{skew} = 1.5ns$  delay on clock pulses arriving at Q3



- Delay on path from Q0 to Q3 is then given by

$$t_{CQ} + 3(t_{AND}) + t_{XOR} + t_{su} - t_{skew} = 6.4 - 1.5 = 4.9ns$$

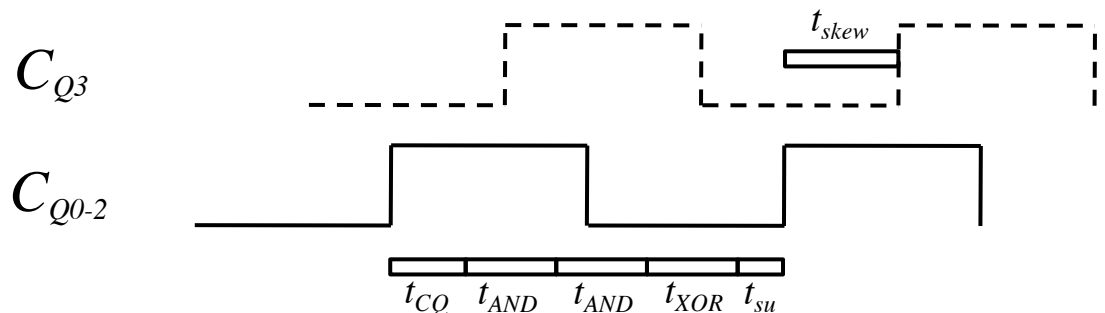since the skew provides additional time before data is loaded into Q3



- However, critical path is now from Q0 to Q2, i.e.

$$\begin{aligned} T_{min} &= t_{CQ} + 2(t_{AND}) + t_{XOR} + t_{su} \\ &= 1.0 + 2(1.2) + 1.2 + 0.6 \\ &= 5.2 ns \end{aligned}$$

$$F_{max} = 192 MHz$$

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

# Negative clock skew

- A negative clock skew, i.e. clock arriving earlier at Q3 than at Q0 – Q2 would have the opposite effect of lengthening the clock period requirement & reducing the maximum clock frequency

Assignment Project Exam Help

<https://tutorcs.com>

WeChat: cstutorcs

# Effect of clock skew on hold times

- As positive clock skew has the effect of delaying the loading of data into FF Q3, it has the effect of increasing the hold time requirement of this FF to  $t_h + t_{skew}$  for all paths that end at Q3
- The shortest such path is from FF Q2 to Q3 and has delay  $t_{cQ} + t_{AND} + t_{XOR} = 0.8 + 1.2 + 1.2 = 3.2 \text{ ns} > t_h + t_{skew} = 1.9 \text{ ns} \therefore$  no violation
- But, when  $t_{skew} = 3.2 - t_h = 2.8 \text{ ns}$ , then hold time violations will exist and the circuit will not work reliably at any frequency
- Good circuit design therefore aims to minimize, if not eliminate, clock skew